

# Verilog

## Why Should I Learn This Language?

- 俗話說得好：“大塊假我以文章”，當硬體發展到VLSI這種“大塊”的地步，以非人力可以處理，故吾人學習寫HDL文章，是不得不的趨勢。




## Different Levels of Abstraction

- **Algorithmic**
  - the function of the system
- **RTL**
  - the data flow
  - the control signals
  - the storage element and clock
- **Gate**
  - gate-level net-list
- **Switch**
  - transistor-level net-list

Verilog-3
 
## Hierarchical structure

- **Represent the hierarchy of a design**



- **modules**
  - the basic building blocks
- **ports**
  - the I/O pins in hardware
  - input, output or inout

Verilog-4

# Modules

**module** module\_name (port\_name);

port declaration

data type declaration

module functionality or structure


**endmodule**

Verilog-5
 
# Examples

- 4-bit adder

```
module add4 (s,c3,ci,a,b)
  port {
    input [3:0] a,b ; // port declarations
    input ci ;
    output [3:0] s : // vector
    output c3 ;
  }
  data type wire [2:0] co ;
  Structure {
    add a0 (co[0], s[0], a[0], b[0], ci) ;
    add a1 (co[1], s[1], a[1], b[1], co[0]) ;
    add a2 (co[2], s[2], a[2], b[2], co[1]) ;
    add a3 (c3, s[3], a[3], b[3], co[2]) ;
  }
endmodule
```




Verilog-6

- A full-adder

```

module add (co, s, a, b, c)
  input a, b, c;
  output co, s;
  xor (n1, a, b);
  xor (s, n1, c);
  nand (n2, a, b);
  nand (n3, n1, c);
  nand (co, n3, n2);
endmodule

```

 

## Sub-module

```

module adder (co,s,a,b,c);
.....
endmodule

```

```

module adder8(...);
  adder add1(c1,s1,a1,b1,1'b0),
        add2(.a(a2),.b(b2),.c(c1),.s (s2)
            ,.co(c2));
.....
endmodule

```

Mapping port positions

Mapping names

## Data Type

- Data type:
  - input : default “ wire”
  - output :

```
module test ( Q,S,clk );
output Q;;
input S,clk;
reg Q;
always@(S or clk or Q)
Q<=(S&clk) ;
endmodule
```

```
dff dff1(D,clk,Q);
```

“wire”

```
always@ (D or clk or Q)begin
Q=(D&clk) | (~clk&Q);
end
```

“ reg ”

Verilog-9

## Gate-Level Modeling

- Net-list description
  - built-in primitives gates
- A full-adder

```
module add (co, s, a, b, c)
```

```
input a, b, c ;
```

```
output co, s ;
```

```
xor (n1, a, b) ;
```


```
xor (s, n1, c) ;
```

```
nand (n2, a, b) ;
```

```
nand (n3,n1, c) ;
```

```
nand (co, n3,n2) ;
```

```
endmodule
```

 


Verilog-10
 
# Verilog Primitives

- Basic logic gates only


- and
- or
- not
- buf
- xor
- nand
- nor
- xnor
- bufif1, bufif0
- notif1, notif0




Verilog-11
 
# Primitive Pins Are Expandable


- One output and variable number of inputs



`nand (y, in1, in2) ;`

 

`nand (y, in1, in2, in3) ;`

 

`nand (y, in1, in2, in3, in4) ;`

- not and buf

- variable number of outputs but only one input

Verilog-12

## Modeling Structures

- Continuous assignment
  - Procedural blocks
    - initial block ( execute only once )
    - always block ( execute in a loop )
- they start together at simulation time-zero

Verilog-13

## Continuous Assignments

- Describe combinational logic
- Operands + operators
- Drive values to a net
  - assign out = a&b ; // and gate
  - assign eq = (a==b) ; // comparator
  - wire #10 inv = ~in ; // inverter with delay
  - wire [7:0] c = a+b ; // 8-bit adder
- Avoid logic loops
  - assign a = b + a ;
  - asynchronous design

Verilog-14

# Operators

{ }	concatenation
+ - * /	arithmetic
%	modulus
> >= < <=	relational
!	logical NOT
&&	logical AND
	logical OR
==	logical equality
!=	logical inequality
? :	conditional

~	bit-wise NOT
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
^~ ~^	bit-wise XNOR
<<	shift left
>>	shift right

Verilog-15

# Operator Precedence

[ ]	bit-select or part-select
( )	parentheses
!, ~	logical and bit-wise negation
&,  , ~&, ~ , ^, ~^, ^~	reduction operators
+, -	unary arithmetic
{ }	concatenation
*, /, %	arithmetic
+, -	arithmetic
<<, >>	shift

>, >=, <, <=	relational
==, !=	logical equality
&	bit-wise AND
^, ^~, ~^	bit-wise XOR and XNOR
	bit-wise OR
&&	logical AND
	logical OR
? :	conditional

Verilog-16



## RTL Statements

- Procedural and RTL assignments
  - reg
  - `out = a + b ;`
- `begin . . . end` block statements
  - group statements
- `if. . . else` statements
- `case` statements
- `for` loops
- `while` loops
- `forever` loops

Verilog-17

## Combinational Always Blocks

- **A complete sensitivity list (inputs)**

```
always @(a or b or c)
    f = a&~c | b&c ;
```

- **Simulation results**

```
always @(a or b)
    f = a&~c | b&c ;
```

- **Parentheses**

```
always @(a or b or c or d)
    z = a + b + c + d ;      // z = (a+b) + (c+d) ;
```

Verilog-18

## Sequential Always Blocks

- Inferred latches (Incomplete branch specifications)


```
module infer_latch(D, enable, Q);  
  input D, enable;  
  output Q;  
  reg Q;  
  always @ (D or enable) begin  
    if (enable)  
      Q <= D;  
  end  
endmodule
```

- the Q is not specified in a branch
  - a latch like 74373

Verilog-19

## Combinational Circuit Design

- Outputs are functions of inputs

 

- Examples


- MUX
- decoder
- priority encoder
- adder

Verilog-20
 
# Multiplexor

- Net-list (gate-level)

```
module mux2_1 (out,a,b,sel) ;  
    output out ;  
    input a,b,sel ;  
    not (sel_, sel) ;  
    and (a1, a, sel_) ;  
    and (b1, b, sel) ;  
    or (out, a1, b1) ;  
endmodule
```



Verilog-21

# Multiplexor

- Continuous assignment

```
module mux2_1 (out,a,b,sel) ;  
    output out ;  
    input a,b,sel ;  
    assign out = (a&~sel)|(b&sel) ;  
endmodule
```

- RTL modeling

```
always @(a or b or sel)  
if(sel)  
    out = b;  
else  
    out = a;
```

Verilog-22

# Multiplexor

- 4-to-1 multiplexor

```
module mux4_1 (out, in0, in1, in2, in3, sel) ;
    output out ;
    input in0,in1,in2,in3 ;
    input [1:0] sel ;
    assign out = (sel == 2'b00) ? in0 :
                (sel == 2'b01) ? in1 :
                (sel == 2'b10) ? in2 :
                (sel == 2'b11) ? in3 :
                1'bx ;
endmodule
```

Verilog-23

```
module mux4_1 (out, in, sel) ;
    output out ;
    input [3:0] in ;
    input [1:0] sel ;
    reg out ;
    always @(sel or in) begin
        case(sel)
            2'd0: out = in[0] ;
            2'd1: out = in[1] ;
            2'd2: out = in[2] ;
            2'd3: out = in[3] ;
            default: 1'bx ;
        endcase
    end
endmodule
```

Verilog-24

## Decoder

- 3-to 8 decoder with an enable control

```

module
    decoder(o, enb_, sel) ;
output [7:0] o ;
input enb_ ;
input [2:0] sel ;
reg [7:0] o ;
always @ (enb_ or sel)
    if(enb_)
        o = 8'b1111_1111 ;
    else

```

```

case(sel)
3'b000 : o = 8'b1111_1110 ;
3'b001 : o = 8'b1111_1101 ;
3'b010 : o = 8'b1111_1011 ;
3'b011 : o = 8'b1111_0111 ;
3'b100 : o = 8'b1110_1111 ;
3'b101 : o = 8'b1101_1111 ;
3'b110 : o = 8'b1011_1111 ;
3'b111 : o = 8'b0111_1111 ;
default : o = 8'bx ;
endcase
endmodule

```

Verilog-25

## Priority Encoder

```

always @ (d0 or d1 or d2 or d3)

```

```

    if (d3 == 1)
        {x,y,v} = 3'b111 ;
    else if (d2 == 1)
        {x,y,v} = 3'b101 ;
    else if (d1 == 1)
        {x,y,v} = 3'b011 ;
    else if (d0 == 1)
        {x,y,v} = 3'b001 ;
    else
        {x,y,v} = 3'bxx0 ;

```

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Verilog-26

# Adder

- RTL modeling

```

module adder(c,s,a,b) ;
output c ;
output [7:0] s ;
input [7:0] a,b ;
    assign {c,s} = a + b ;
endmodule
    
```

- Logic synthesis


- CLA adder for speed optimization
- ripple adder for area optimization

# Procedural Assignments

- Blocking assignments

```

 
always @(posedge clk) begin
    rega = data ;
    regb = rega ;    regat=data
                    regbt=data
end
    
```




- Non-blocking assignment:

```

 always @(posedge clk) begin
    regc <= data ;
    regd <= regc ;
end
                    regct=data
                    regdt=regct-1
    
```



# Sequential Circuit Design

 

- a feedback path
- the state transition
  - synchronous circuits
  - asynchronous circuits

Verilog-29

- **Examples**

- D flip-flop
- D latch
- register
- shifter
- counter
- pipeline
- FSM

Verilog-30

# Flip-Flop

- Synchronous clear

```
module d_ff (q,d,clk,clr_) ;  
    output q ;  
    input d,clk,clr_ ;  
    reg q ;  
    always @ (posedge clk)  
        if (~clr_) q = 0 ;  
        else      q = d ;  
endmodule
```

- Asynchronous clear

```
always @ (posedge clk or negedge clr_)  
    if (~clr_) q = 0 ;  
    else      q = d ;
```

Verilog-31

# Register

```
module register (q,d,clk,clr_, set_) ;  
    output [7:0] q ;  
    input [7:0] d ;  
    input clk,clr_, set_ ;  
    reg [7:0] q ;  
    always @ (posedge clk or negedge clr_ or negedge set_)  
        if (~clr_)  
            q = 0 ;  
        else if (~set_)  
            q = 8'b1111_1111 ;  
        else  
            q = d ;  
endmodule
```

Verilog-32



## D Latches

- D latch

```
always @ (enable or data)
```

```
  if (enable)
```


```
    q = data ;
```

- D latch with gated asynchronous data

```
always @ (enable or data or gate)
```

```
  if (enable)
```


```
    q = data & gate
```

 

Verilog-33
 
## Shifter


```
module shifter (so,si,d,clk,ld_,clr_) ;
output so ;
input [7:0] d ;
input si,clk,ld_,clr_ ; // asynchronous clear and synchronous
load
reg [7:0] q ;
assign so = q[7] ;
always @ (posedge clk or negedge clr_)
  if (~clr_)
    q = 0 ;
  else if (~ld_)
    q = d ;
  else
    q[7:0] = {q[6:0],si} ;
endmodule
```




Verilog-34

# Finite State Machine

- Moore model

 

- Mealy model

 


Verilog-35

# Inefficient Description

```
module count (clock, reset, and_bits, or_bits, xor_bits);
input clock, reset;
output and_bits, or_bits, xor_bits;
reg and_bits, or_bits, xor_bits;
reg [2:0] count;
always @(posedge clock) begin
    if (reset)
        count = 0;
    else
        count = count + 1;
        and_bits = & count;
        or_bits = | count;
        xor_bits = ^ count;
end
endmodule
```

Verilog-36

- Six implied registers

 

Verilog-37

## Efficient Description

- Separate combinational and sequential circuits

```


module count (clock, reset,
  and_bits, or_bits, xor_bits);
input clock, reset;
output and_bits, or_bits,
  xor_bits;
reg and_bits, or_bits, xor_bits;
reg [2:0] count;
always @(posedge clock) begin
  if (reset)
    count = 0;
  else
    count = count + 1;
end
endmodule

// combinational circuits
always @(count) begin
  and_bits = & count;
  or_bits = | count;
  xor_bits = ^ count;
end
endmodule

```


Verilog-38

- Three registers are used

 


Verilog-39

## Pipelines

 

- An example

 

```

assign n_sum = a+b
assign p = sum * d_c
// plus D flip-flops
always @ (posedge clk)
    sum = n_sum ;

```

Verilog-40

# Memory

```
module memory (data, addr, read, write);
    input read, write;
    input [4:0] addr;
    inout [7:0] data;
    reg [7:0] data_reg;
    reg [7:0] memory [0:8'hff];
    parameter load_file = "cput1.txt";
    assign data = (read) ? memory [addr] : 8'hz;
    always @ (posedge write)
        memory[addr] = data;
    initial
        $readmemb (load_file, memory);
endmodule
```